

6 DI Proporation


3.1

Pwm function code and graph:

```

1  function v = pwm(t,T,d)
2  figure(1);
3  for i = 1:length(t)
4    pos = mod(t(i),T);
5    if(pos >= d)
6      v(i) = 0;
7    else
8      v(i) = 1;
9    end
10   end
11   plot(t,v)
12   end

```

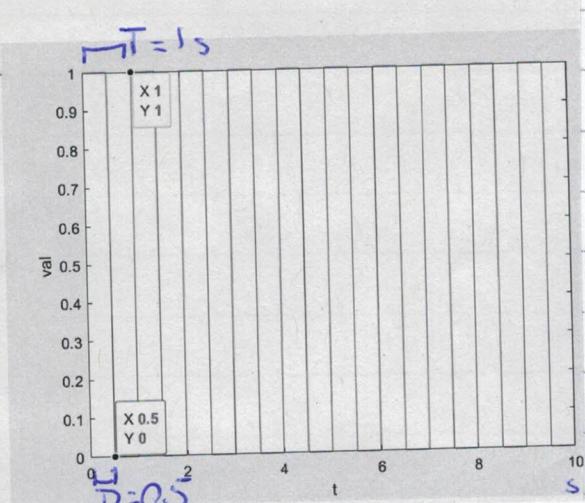


3.2

Discontinuons mode

We assume current falls to 0 in same point when it is in off-mode state.

Timing graph:

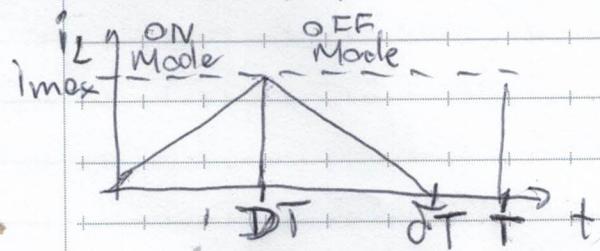

Signed by Originator

Small Print

Print Name rofeng@vdi.han Date

Signed by Witness

Small Print

Print Name rofeng@vdi.han Date

On mode:

$$\frac{i_{max}}{dt} = \frac{V_{in}}{L}, \text{ so } i_{max} = \frac{d + V_{in}}{L} = \frac{DT V_{in}}{L}$$

Off mode:

$$L \frac{i_{max}}{dt} = V_{in} - V_{out}$$

$$i = \frac{V_{in} - V_{out} \cdot dt}{L}$$

$$\Phi_m i_{max} + \frac{(V_{in} - V_{out}) \cdot DT}{L} = 0$$

$$DT V_{in} + (V_{in} - V_{out}) DT = 0$$

$$DT V_{in} + DT V_{in} - DT V_{out} = 0$$

$$DT = \frac{DV_{in}}{V_{out} - V_{in}}$$

We can calculate average i_{load} since it is diode during off state.

$$i_{load} = \frac{i_{max}}{2} \cdot DT \cdot \frac{1}{T} = \frac{DT V_{in}}{2L} \cdot \frac{DV_{in}}{V_{out} - V_{in}}$$

$$V_{load} = V_0 = \frac{i_{load}}{R}$$

$$V_{out} = \frac{D^2 V_{in}^2 T R}{2L(V_{out} - V_{in})R}$$

$$(2LR V_{out} - 2LV_{in} V_{out}) V_{out} = D^2 V_{in}^2 T R$$

$$2LR V_{out}^2 - 2LV_{in} V_{out} = D^2 V_{in}^2 T R$$

$$2LR V_{out}^2 - 2LR V_{in} V_{out} - D^2 T V_{in}^2 R = 0$$

$$V_{out} = \frac{2LR V_{in} \pm \sqrt{4L^2 R^2 V_{in}^2 + 4LR D^2 T V_{in}^2}}{4LR} = \frac{2LR V_{in} \pm \sqrt{4LR V_{in}^2 (LR + D^2 T)}}{4LR} =$$

$$= (V_{out} - V_{in}) V_{out} = \frac{D^2 V_{in}^2 T R}{2L}$$

$$V_{out}^2 - V_{in}V_{out} - \frac{D^2 V_{in}^2 TR}{2L} = 0$$

$$V_{out} = \frac{V_{in} \pm \sqrt{V_{in}^2 + \frac{2D^2 TR}{L} V_{in}^2}}{2} = \frac{V_{in} \pm V_{in} \sqrt{1 + \frac{2D^2 TR}{L}}}{2}$$

$V_{out} > V_{in}$ so

$$V_{out} = \frac{V_{in} + V_{in} \sqrt{1 + \frac{2D^2 TR}{L}}}{2}$$

State space form switch closed

$$\frac{d}{dt} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} = \begin{bmatrix} AB \\ CD \end{bmatrix} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} + \begin{bmatrix} E \\ F \end{bmatrix} V_{in}$$

$$\frac{d}{dt} i_L = A \cdot i_L + B \cdot V_{out} + E \cdot V_{in}$$

$$\frac{d}{dt} V_{out} = C \cdot i_L + D \cdot V_{out} + F \cdot V_{in}$$

$$\frac{d}{dt} i_L = \frac{V_{in}}{L}, \text{ so } A=0, B=0, E=\frac{1}{L}$$

$$\frac{d}{dt} V_{out} = -\frac{V_{out}}{RC}, \text{ so } C=0, D=-\frac{1}{RC}, F=0$$

$$\frac{d}{dt} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_{in}$$

switch opened diode forward region

$$\left\{ \begin{array}{l} L \frac{di}{dt} = V_{in} - V_{out} \Leftrightarrow \frac{di}{dt} = \frac{1}{L} V_{in} - \frac{1}{L} V_{out} \\ \frac{dV_{out}}{dt} = \frac{1}{C} i_L - \frac{V_{out}}{CR} \end{array} \right.$$

$$\frac{d}{dt} \begin{bmatrix} \frac{di}{dt} \\ \frac{dV_{out}}{dt} \end{bmatrix} = \begin{bmatrix} 0 & \frac{-1}{L} \\ \frac{1}{C} & \frac{-1}{CR} \end{bmatrix} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} + \begin{bmatrix} \frac{1}{L} V_{in} \\ 0 \end{bmatrix}$$

switch opened, diode in reverse region

$$\frac{di}{dt} = 0 \quad \frac{dV_{out}}{dt} = \frac{-V_{out}}{CR}$$




$$\frac{d}{dt} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & \frac{-1}{CR} \end{bmatrix} \begin{bmatrix} i_L \\ V_{out} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} V_{in}$$

4.4

V _{in}	1.5
R	680 Ω
C	200 μF
L	180 μH

$$d = 0.3$$
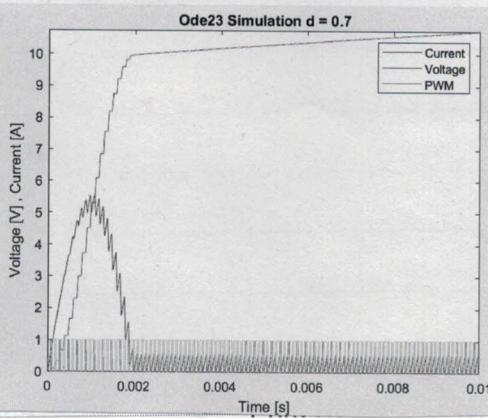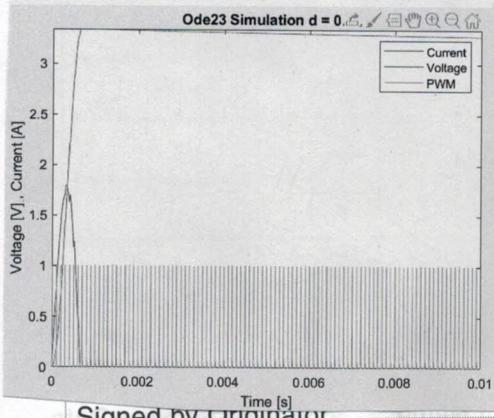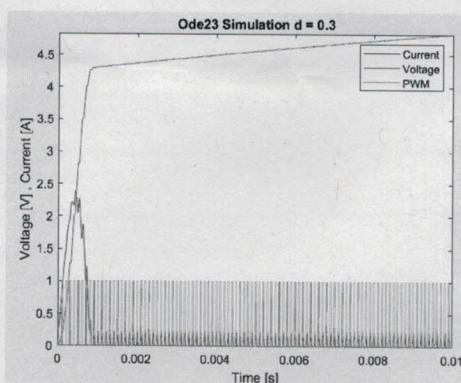
```
function dx=boost(t,x)
global v_in R C L T d
dx=zeros(2,1);
if pwm(t,T,d)==1
dx(1) = v_in/L;
dx(2) = -x(2)/(R*C);
end
if pwm(t,T,d)==0 && x(1)>=0
dx(1) = -x(2)/L+v_in/L;
dx(2) = x(1)/C-x(2)/(C*R);
end
if pwm(t,T,d)==0 && x(1) <0
dx(1) = 0;
dx(2) = -x(2)/(C*R);
end
```



Signed by Originator

Date


Signed by Witness

Print Name

Date


$D=0.1$	$T=124e^{-5}$	3.3 V
$D=0.3$	$T=8e^{-5}$	4.3 V
$D=0.5$	$T=4.8e^{-5}$	6 V
$D=0.6$	$T=0.5e^{-5}$	7.4 V
$D=0.8$	$T=3e^{-5}$	14 V

max $T =$

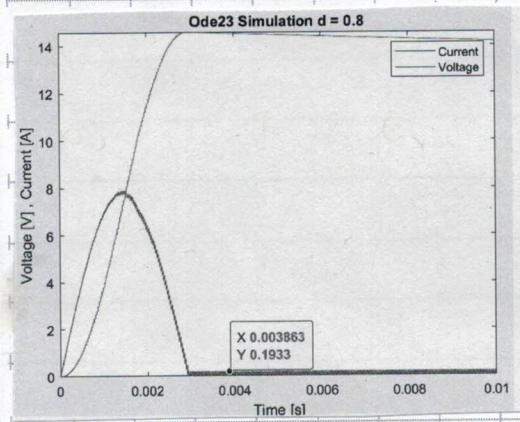

Assumptions are valid,
the current remains
nearly 0.2 A and
it matches my previous
calculations.

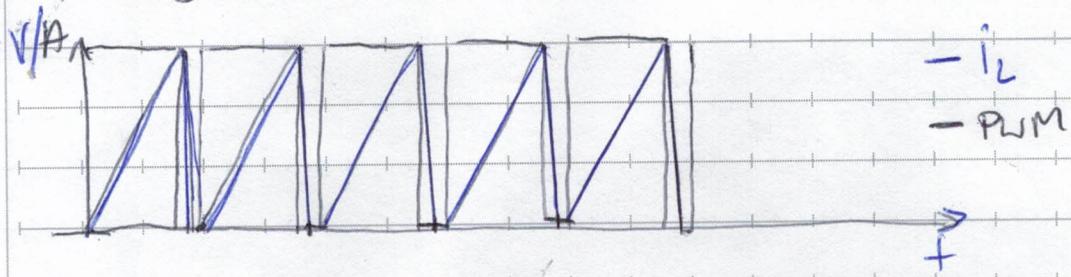The above example work in discontinuous mode
during stable state!



$$Y = \frac{(R_2 + R_1)R_{dummy}}{R_1 + R_2 + R_{dummy}} = 663.11 \Omega$$

$$R_{dummy} = 680 \Omega \quad R_{dummy} - \frac{Y}{R_{dummy}} \cdot 100\% = 2,48\%$$

The value of total resistance has changed only
by 2.48%. It is not significant value and
that change won't influence on circuit's behaviour.

Signed by Originator *smekl4199*

Print Name *toleright@vdi.han.de* Date

Signed by Witness *smekl4199*

Print Name *smekl4199* Date

15

The complete cse section of dynamic simulator code:

```


switch casel
    case 1
        %Case: Switch open and diode reverse biased
        dVout_dt= -Vout/(R*C);
        Vout=Vout+dVout_dt*timeStep; %Update Vout with new value
        dIL_dt=0;

    case 2
        %Case: Switch open, diode forward biased

        dIL_dt= -Vout/L+Vin/L;
        dVout_dt = iL/C-Vout/(C*R);
        iL=iL+dIL_dt*timeStep; %Update iL with new value
        Vout=Vout+dVout_dt*timeStep; %Update Vout with new value


    case 3
        %Case: switch closed
        dVout_dt= -Vout/(R*C);
        Vout=Vout+dVout_dt*timeStep;
        dIL_dt = Vin/L;
        iL=iL+dIL_dt*timeStep;
end

```

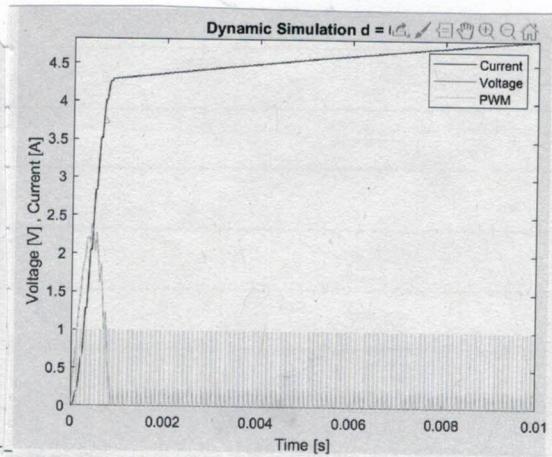

Dynamic simulations for different k_p and V_{target} values

$K = 0.01$

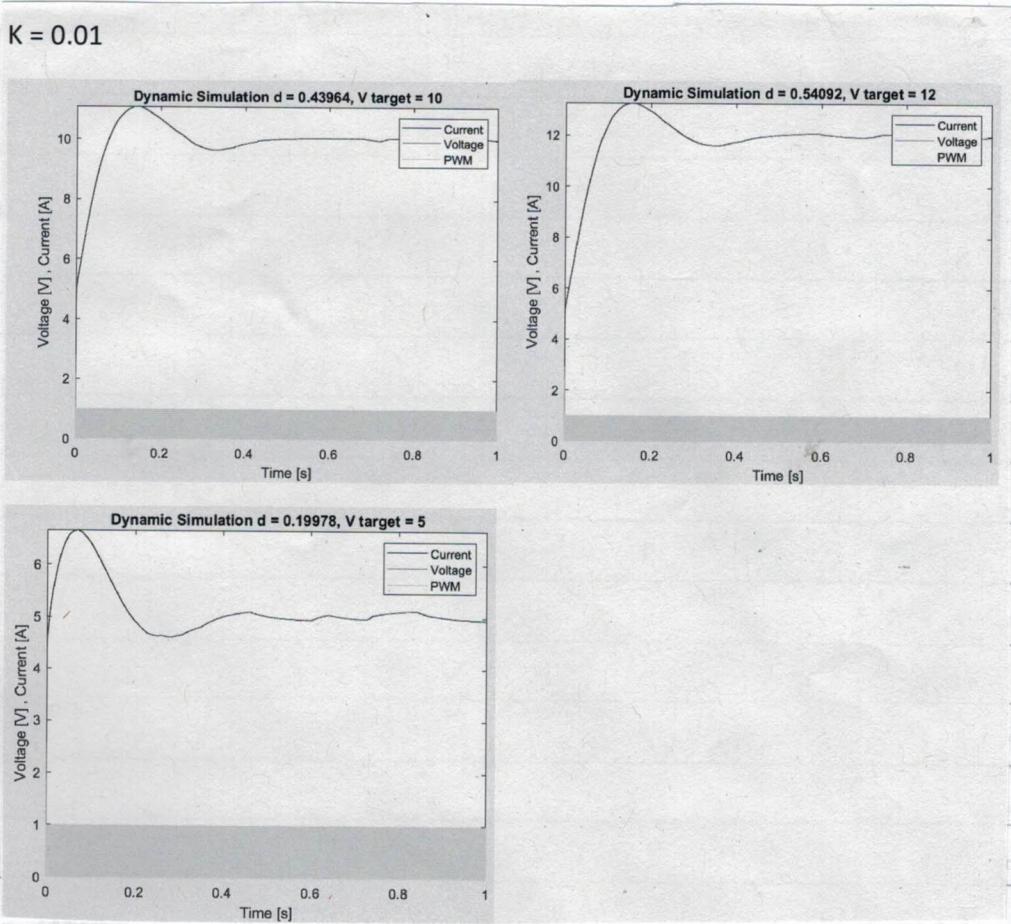

Signed by Originator

email to be filled

Print Name







10/10/2019 Date

Signed by Witness

email to be filled

Print Name

10/10/2019 Date

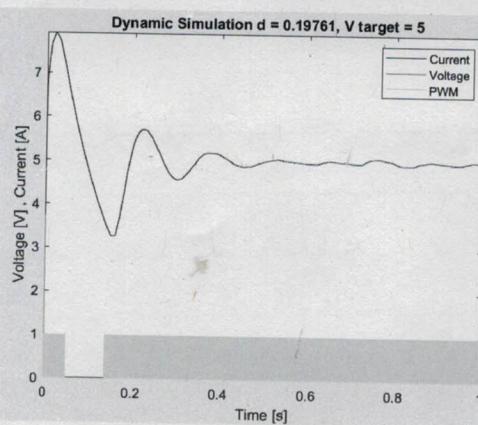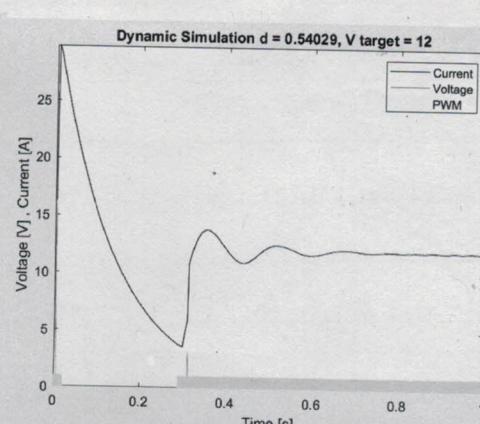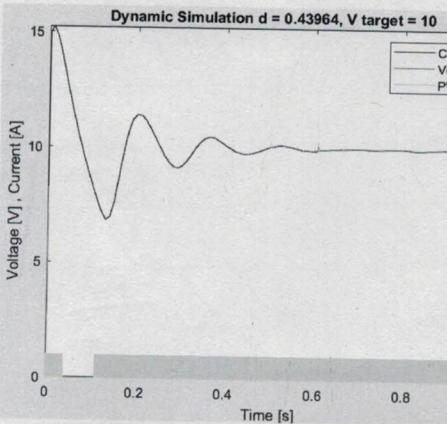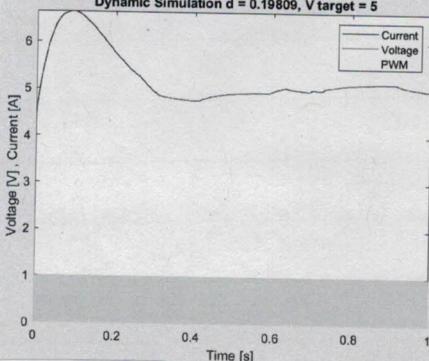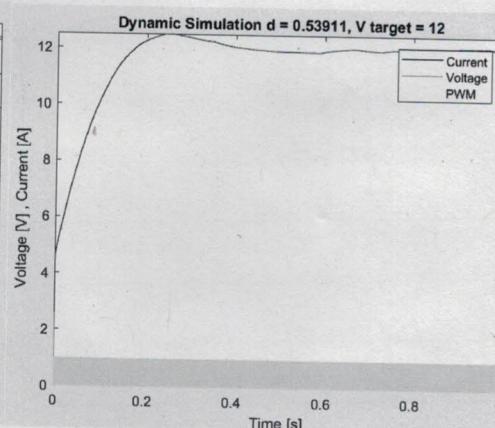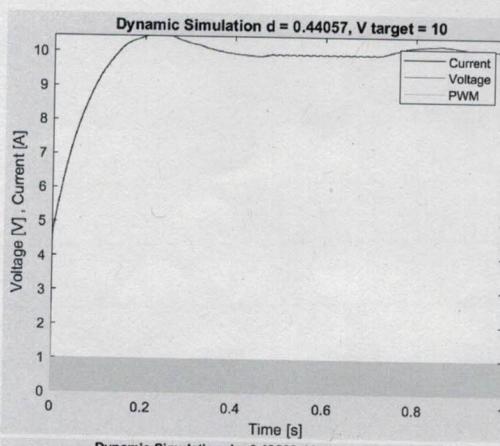K=0.05**K = 0.005**Signed by Originator smk1193Print Name rotaright@vuhome Date _____Signed by Witness smk1193Print Name rotaright@vuhome Date _____

The S.3 Options


PID Controller

control function:

$$u(t) = K_p e(t) + K_i \int_0^t e(t') dt' + K_d \frac{de(t)}{dt}$$

proportionell term
integrel term
diferentiel term

PID implementation in dynamic simulator:

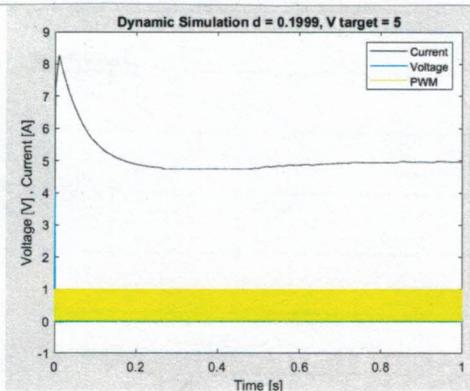

This is improved simulation for target 5 V. In previous proportional controller the simulation reaches stable state in 0.5 s while in PID controller it is much quicker and less 0.2 s.

To achieve good controller stability it is necessary to get K_p, K_i, K_d values the best values.

There is stable which describe effects of increasing parameter independently:

Parameter	Rise time	Overshoot	Settling time	Steady-state error	Stability
K_p	Decrease	Increase	Small change	Decrease	Decrease
K_i	Decrease	Increase	Increase	Eliminate	Decrease
K_d	Small change	Decrease	Decrease	—	Improves, if K_d small

wikipedia.org ext
entry: PID controller

Current limiter:


if ($i_L > i_{limit}$)

$$i_{error} = i_L - \text{current } i_{limit};$$

$$kPi = 0.0001;$$

$$\text{dutyCycle} = \text{dutyCycle} - i_{error} * kPi;$$

end

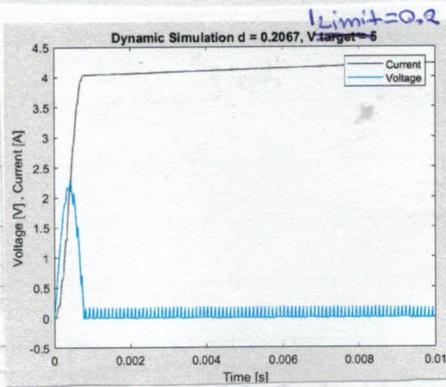

SI

Lab Code:	None	Poor	OK	Good	Exceptional	Outstanding
Preparation	0	1	2	3	4	5
Progress	0	1	2	3	4	5
Understanding	0	1	2	3	4	5
Logbook Use	0	1	2	3	4	5

Demonstrators only

Print Full Name Tancharoen R Signed TH

Signed by Originator emelij1109

Print Name rotanich@vdbond Date _____

Signed by Witness emelij1109

Print Name rotanich@vdbond Date _____